


Aug-24


Carry Lookahead Adder

Stage 1:

C_1
 \vdots → Chunk
 C_8 1...8


Compute the G, P functions for larger sequences of bits in a tree fashion.

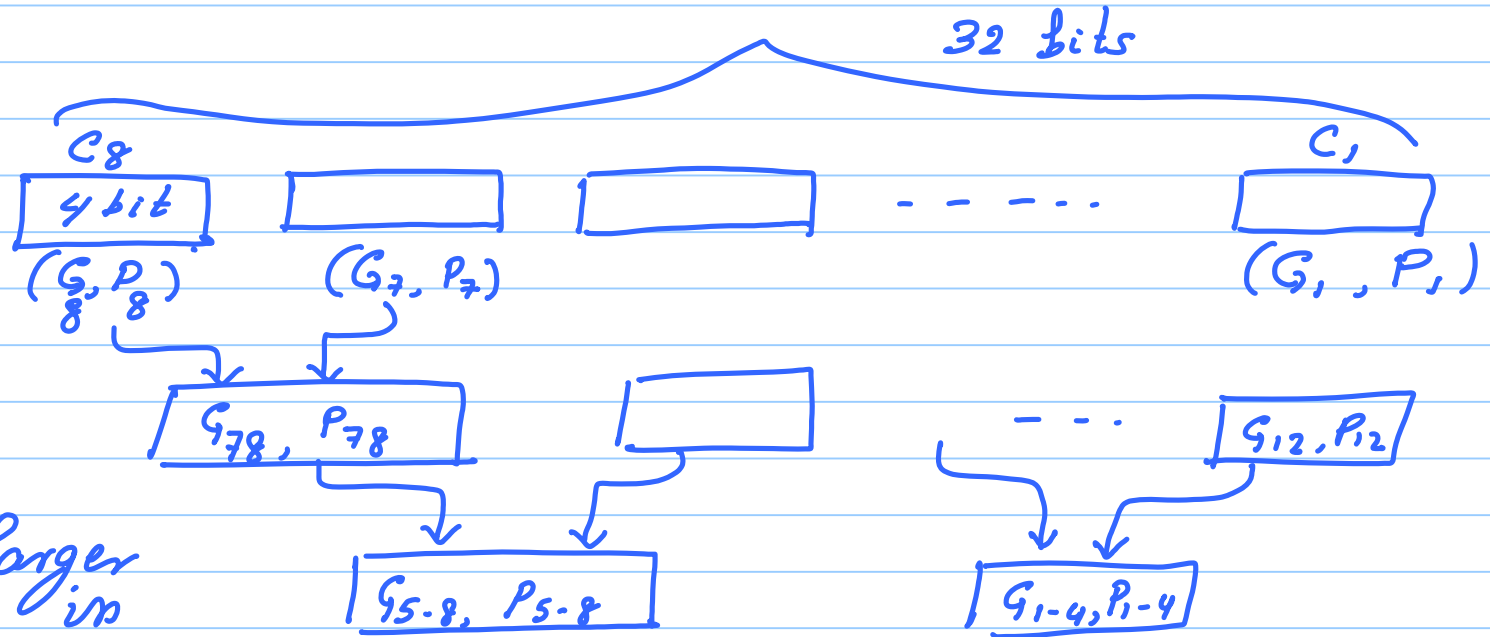

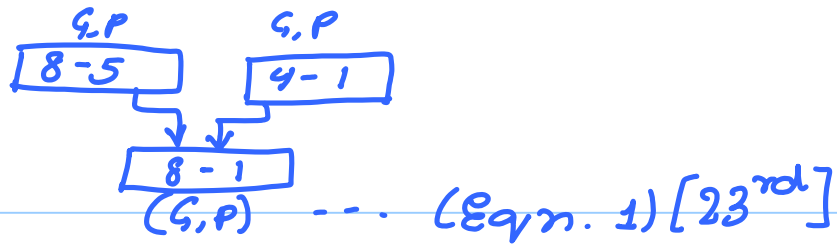

Stage 2

last level

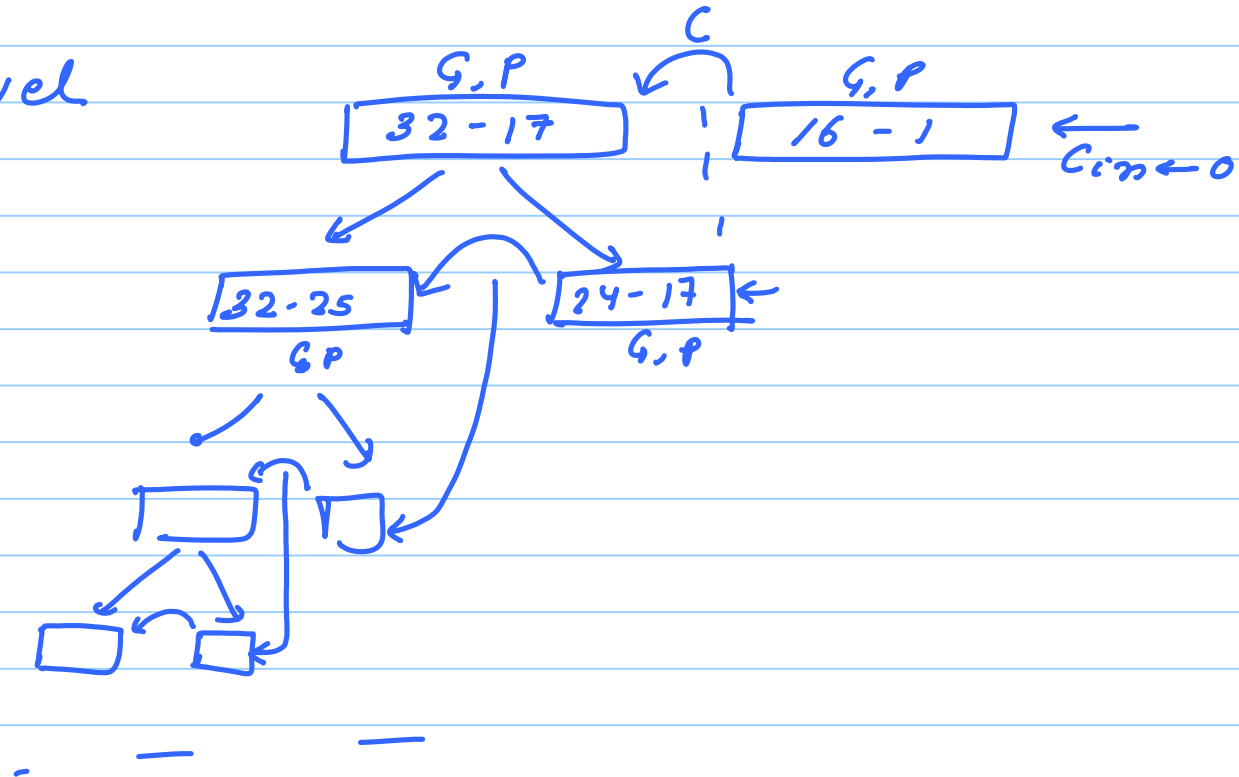

Stage 3

Generate final result.


Time

Stage 1: Successively compute B.P for
 $O(\log(n))$ larger & larger chunks

Stage 2: Compute the C_{in} values to every
 $O(\log(n))$ chunk by traversing the tree from
the root to the leaves

Stage 3: Do the final addition in each
 $O(1)$ chunk & compute result

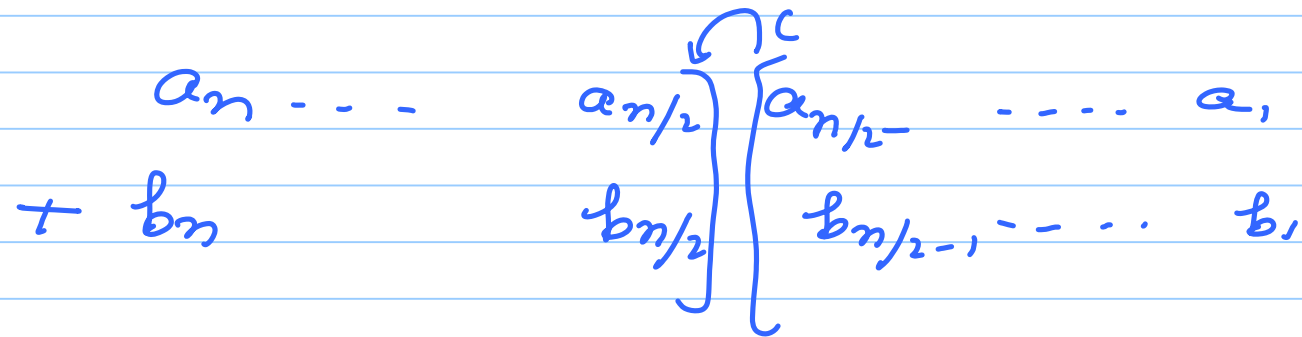
Total time taken: $O(\log(n))$
[fastest possible ladder]



Two independent sub problems

Multiplication.

(unsigned positive numbers)

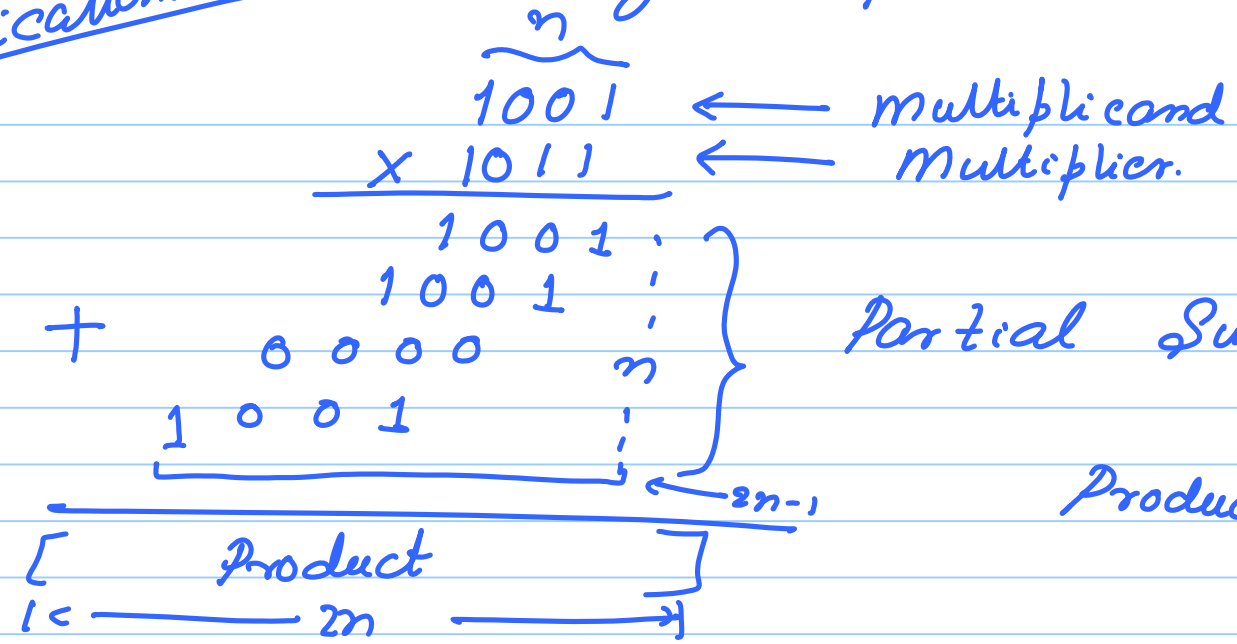


Partial Sum.

Product = \sum Partial Sum

Simple algorithm: Add the n partial sum.
 Sequential addition $O(n \log(n))$ time.

Slightly smarter (tree multiplier)

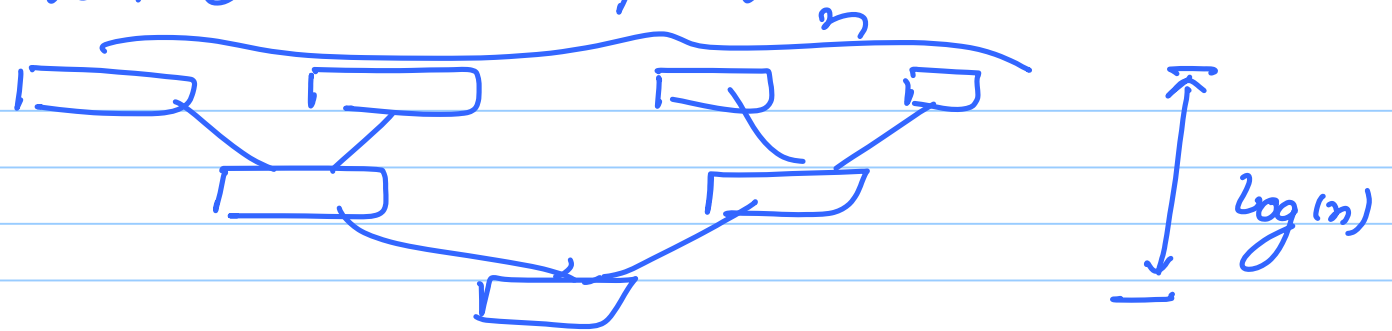

$$\begin{aligned} \text{Total time: } & \# \text{ levels} \times (\text{Time per level}) \\ & = O(\log(n) \times \log(n)) \\ & = O((\log(n))^2) \end{aligned}$$

Aim: Multiply in $O(\log(n))$ time.

✓ New kind of adder: Carry Save Adder (CSA)

CSA:

$$A + B + C = D + E$$

$$\begin{array}{r} \textcircled{A} \ 1000 \dots (8) \\ \textcircled{B} \ 0101 \dots (5) \\ \textcircled{C} \ 1011 \dots (11) \\ \hline 0110 \leftarrow D \\ 1001 \leftarrow E \end{array} \quad \begin{array}{l} + \\ + \end{array} \begin{array}{l} \rightarrow \\ \rightarrow \end{array} 24$$

$$\left\{ \begin{array}{l} D = 0110 \dots (6) \\ E = 10010 \dots (18) \end{array} \right\} \begin{array}{l} + \\ + \end{array} \rightarrow 24$$


How long does a CSA take to compute

$$A + B + C = D + E$$

It takes $O(1)$ time

(No dependence across bits)

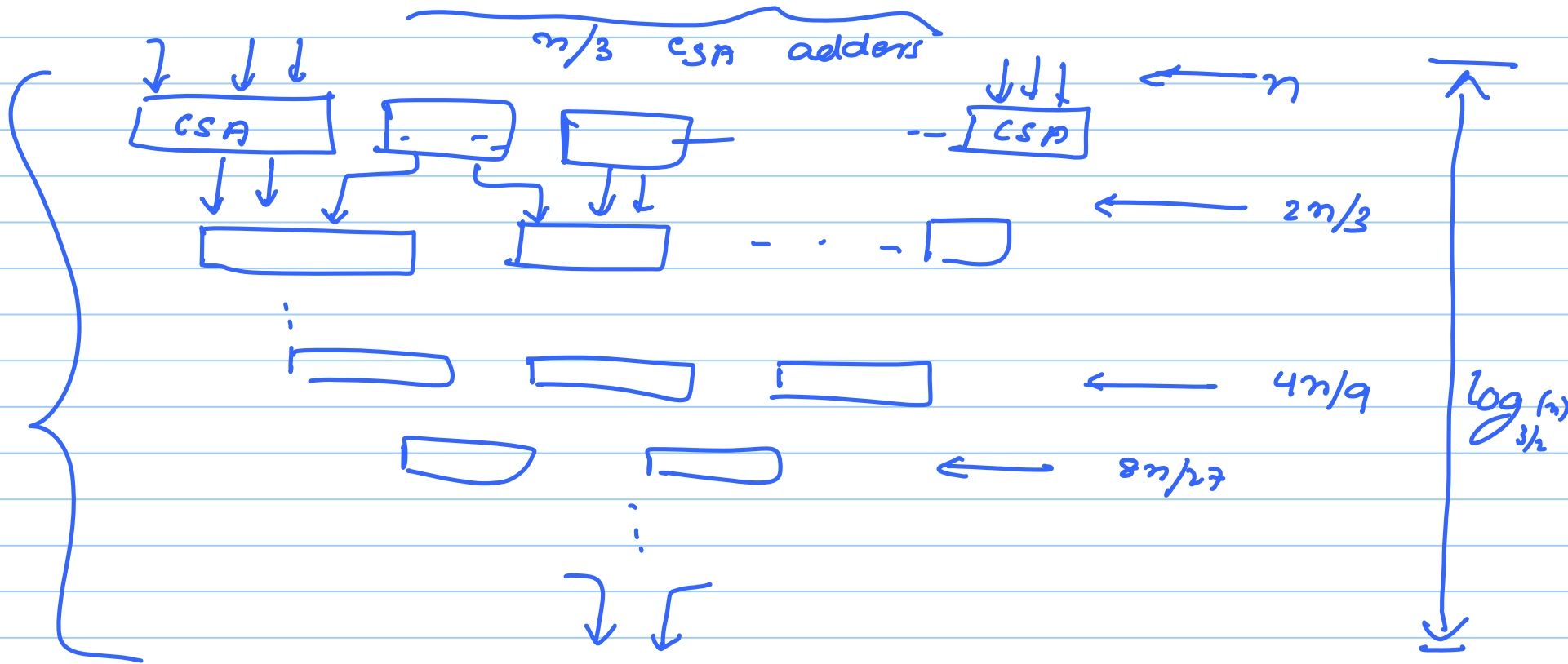Problem of Multiplication: n independent partial sums need to be added



levels : $O(\log_{3/2} n) \leftrightarrow O(\log(n))$

Time per level: $O(1)$

All CSAs in one level operate parallelly

Stage 1.

$$\underbrace{P_1 \quad - \quad - \quad + \quad P_2}_{\text{Partial Sums}} = \underbrace{P_1' + P_2'}_{2 \text{ nums}}$$

Total Time (Stage 1) = $O(\log(n))$

Stage 2

$$\text{Product} = \underbrace{P_1' + P_2'}_{\text{CLA}} \Rightarrow O(\log(n))$$

$$\text{Total time: } O(\log(n)) + O(\log(n)) = \boxed{O(\log(n))}$$

Technology that we used:

Wallace Tree
Multiplier.

$$O(\log(n))$$

+

$$O(\log(n))$$

CLA

$$= O(\log(n))$$




CSA \rightarrow Carry Save
Adder

CLA \rightarrow Carry Lookahead
Adder.

Extension

Problem: Add m (n -bit) numbers.

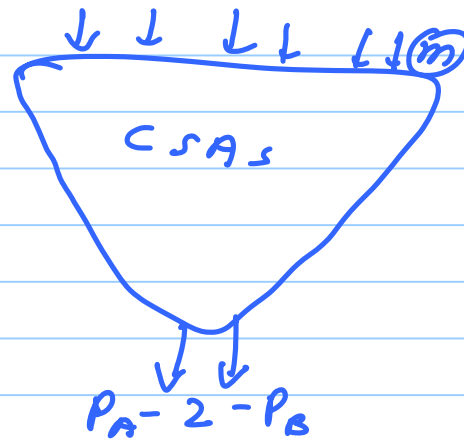

$O(\log(m))$

Time (stage_i) = $O(\log(m))$

Every level the size of the

output is at max. 1 bit more than

the size of the input.

$$\log(P_n) \leq n + \log(m)$$

$$\log(P_s) \leq n + \log(m)$$

Time (Stages)

$P_A + P_B = \text{result}$
(CPU)

$$O(\log(n + \log m))$$

$$\text{Total Time: } O[(\log m) + \log(n + \log m)]$$

Next Class

Division (slow)
(unsigned)

Division when the sign of dividend & divisor is not the same.

$$-7/3$$

$$\textcircled{1} \quad -7 = 3 \times (-2) + (-1)$$

$$\textcircled{2} \quad -7 = 3 \times (-3) + 2$$

Homework

1) Q.1

a) Write the algo. in C
→ read input files

b) arm-elf-gcc -S file.c

c) file.s



1) open

2) reduce instructions

Do not touch the line that contain directives

.align .word
.glob .LCO

2) Process is same.

2x 160 bit nums